

# Design of a 4-Bit Sequence Detector

FSM in VHDL – Nexys 4 DDR  
Implementation  
Tanner Roberson

# Project Requirements

- Detect user-defined 4-bit sequence using FSM
- Allow overlap
- VHDL behavioral modeling in AMD Vivado
- Generalized FSM (not hardcoded)
- Test bench for all 16 sequences
- Implement on Nexys 4 DDR:
  - SW0: Clock, SW1: Input w
  - SW5–SW2: Target sequence
  - CPU Reset: Reset
  - LD0: Output z

# Learning Objectives

- Build sequence detector FSM for any 4-bit sequence
- Design and simulate VHDL test bench
- Practice behavioral modeling
- Learn generalized FSM design
- Implement and test on FPGA

# General Approach

1. Define FSM states
2. Write behavioral VHDL FSM logic
3. Implement reset
4. Create test bench for all sequences
5. Verify with waveforms
6. Deploy on FPGA


# FSM Design Details

- Shift inputs into 4-bit register each cycle
- FSM checks if input == target sequence
- Output z=1 on match
- Overlap handled via transitions
- Reset returns to beginning state

# Example State Diagram (1010)

Target sequence: 1010

Start/Reset

 


# Example State Table (1010)

Current State	Input (W)	Next State	Output (Z)
A	0	A	0
	1	B	0
B	0	A	0
	1	C	0
C	0	D	0
	1	C	0
D	0	A	0
	1	E	0
E	0	A	1
	1	C	1
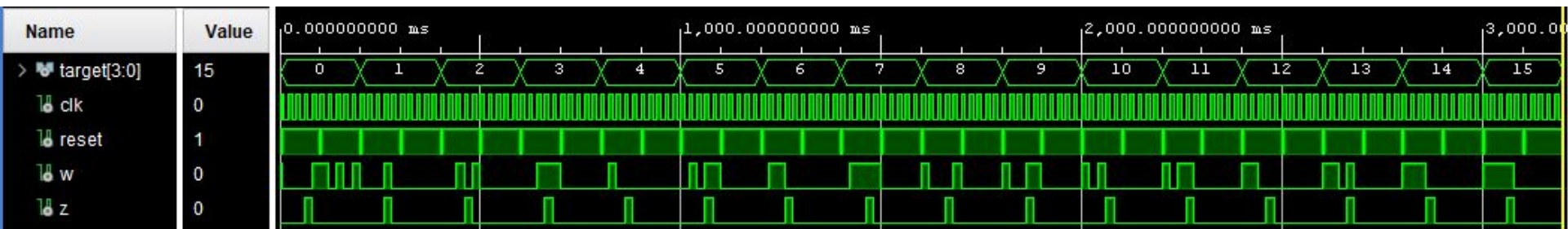
# Simulation Results

- 10 inputs per sequence
- 5 correct  $\rightarrow z=1$  at 4th input
- 5 incorrect  $\rightarrow z=0$





# FPGA Implementation

- Nexys 4 DDR connections:
- SW0: Clock
- SW1: Input w
- SW5–SW2: Target sequence
- Reset: CPU Reset
- LD0: Output z

# Observations & Challenges

- Concurrent VHDL statements caused 1-cycle delay
- Solution: store last 3 inputs in shift register
- FSM generalized for all 16 sequences

# Summary & Takeaways

- Designed generalized FSM sequence detector
- Verified with simulation waveforms
- Implemented on Nexys 4 DDR FPGA
- Learned FSM overlap handling, VHDL modeling, test benching, FPGA deployment